

UGANDA MARTYRS UNIVERSITY

UNIVERSITY EXAMINATIONS

FACULTY OF SCIENCES

DEPARTMENT OF NATURAL

SEMESTER 1, 2023/24 FINAL ASSESSMENT

ELECTRONICS II

DATE : 15/12/2023

TIME : 8:00 - 5:00PM

DURATION: 3 Hrs

Instructions

1. Carefully read through *ALL* the questions before attempting.
 2. The examination has a total of eight (8) questions. ANSWER FIVE (5) Questions
(All questions carry equal marks).
 3. Ensure that your **Reg. number Name and Programme of study** are indicated on all pages of your work.
 4. Ensure that your work is **clear and readable**. Untidy work will be penalized.
 5. Any type of examination Malpractice will lead to automatic disqualification.
-

Where necessary Assume:

Electron charge e	=	$1.6 \times 10^{-19} \text{C}$
Permittivity of free space ϵ_0	=	$8.85 \times 10^{-12} \text{Fm}^{-1}$
Speed of light in a vacuum c	=	$3.0 \times 10^8 \text{m/s}$
Permeability of free space μ_0	=	$4\pi \times 10^{-7} \text{Hm}^{-1}$
Boltzmann's constant k	=	$1.4 \times 10^{-23} \text{JK}^{-1}$
Planck's constant h	=	$6.6 \times 10^{-34} \text{JS}$
Avogadro's number N_A	=	$6.02 \times 10^{23} (\text{mole})^{-1}$
Universal gas constant R	=	$8.31 \text{JK}^{-1} \text{mole}^{-1}$
Gravitational constant G	=	$6.67 \times 10^{-11} \text{Nm}^2 \text{kg}^{-2}$
Electron mass m	=	$9.11 \times 10^{-31} \text{kg}$
Acceleration due to gravity, g	=	9.8ms^{-2}

Question 1

- a) i) How do you understand with the term field effect transistor. (1mk)
- ii) Mention the main types of field effect transistors. (1mk)
- iii) Describe the major composition of junction field effect transistor. (2mks)
- b) i) With aid of labeled diagram, explain the working of n- type junction field effect transistor. (5mks)
- ii) Sketch an I-V out-put characteristics of n- type junction field effect transistor and indicate on it Ohmic region, pinch off line and saturation region. (3mks)
- c) An n- channel JFET with saturation current $I_{DSS} = 6 \text{mA}$ and pinch off voltage $V_p = -6 \text{V}$ is used in the self-bias circuit of figure 1. Given that $V_{DD} = 12 \text{V}$, $R_D = 1.5 \text{k}\Omega$ and $R_S = 500 \Omega$. Determine the operating point (determine I_D , V_{DS} , V_{GS}) (8mks)

S

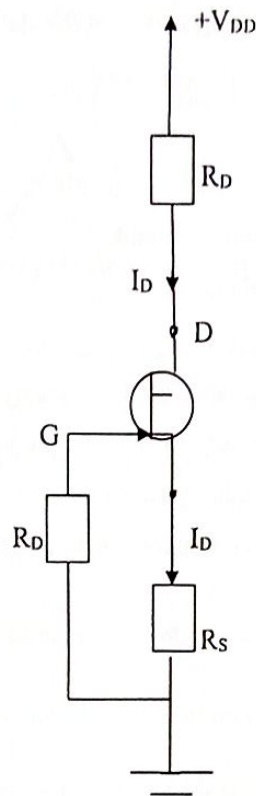


Fig. 1

Question 2

- 2 a) i) Distinguish between cut off and pinch off voltage. (2mks)
- ii) Identify the major types of metal oxide semi-conductor field effect transistor (MOSFET) (2mks)
- iii) State the common metal oxide used in MOSFET to separate the gate and the channel. (1mk)
- b) i) with aid of a diagram explain the working of depletion mode MOSFET. (5mks)
- ii) Sketch I-V transfer characteristic for enhancement mode n-MOSFET. (2mks)
- iii) Define the term threshold voltage as applied in MOSFET. (1mk)
- iv) How does the threshold voltage vary in the different MOSFET. (2mks)
- c) Given that the drain current I_D of a JFET in absence of gate current is a function of V_{GS} and V_{DS} ,
 - i) Write down the changes in I_D (2mks)

ii) Suppose $\delta I_D = i_d$, $\delta V_{GS} = V_{gs}$ and $\delta V_{DS} = V_{ds}$, write the small- signal equivalent circuit equation hence define the major variables in the equation. (3mks)

Question 3

- a) i) How do you understand the term resonance circuit. (1mk)
- b) i) identify any two application of tuned circuit. (1mk)
- ii) State the two types of resonators. (1mk)
- iii) Explain how the performance of oscillator circuit can be improved. (2mks)
- iv) Mention the fundamental parameter used to describe the behavior of RLC circuit. (1mk)
- v) Distinguish between bandwidth and quality factor. (2mks)
- c) A series RLC circuit has the following components $R = 100\Omega$, $L = 10mH$ and $C = 25nF$. Calculate the following parameters;

- i) Resonance frequency. (2mks)
- ii) Damping factor. (2mks)
- iii) Band width. (2mks)
- iv) Q- factor. (2mks)
- d) The figure 2 shows a resonant circuit

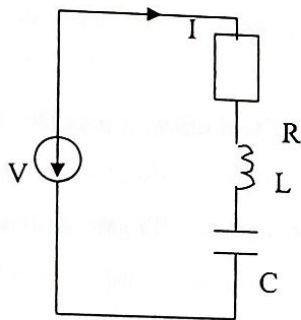


Figure 2

Determine a second order differential equation for the voltage in the circuit at any time; also determine the maximum current of the amplitude of current for the circuit. (4mks)


Question 4

- a) i) what is a filter. (1mk)
- ii) Distinguish the major categories of filters. (2mks)

- b) i) Define the four common filters you know. (4mks)
- ii) Draw the frequency response of any two of the filters defined in b (i). (4mks)
- c) i) Define the term voltage transfer function. (1mk)
- ii) With reference to low pass filter, derive the voltage transfer function. (3mks)
- iii) A low pass filter circuit consisting of resistor of $4.7\text{ k}\Omega$ in series with a capacitor of 47 nF is connected across 10 v sinusoidal supply. Calculate the output voltage and the voltage transfer function at a frequency of 100 Hz . (Take $Z_C = \frac{1}{2\pi f C}$) (5mks)

Question 5

- a) i) Define the term operational amplifier. (1mk)
- ii) Draw a well labeled circuit symbol of an operational amplifier. (3mks)
- b) i) Explain the major characteristics of ideal operational amplifier. (6mks)
- ii) When is an operational amplifier said to be inverting or non-inverting. (2mk)
- c) i) with reference to an inverting operational amplifier, show that the differential $gain = \frac{-R_F}{R_{in}}$ (3mks)
- ii) Given an inverting operational amplifier below with an input voltage of 10 mv , determine the differential gain and output voltage. (5mks)

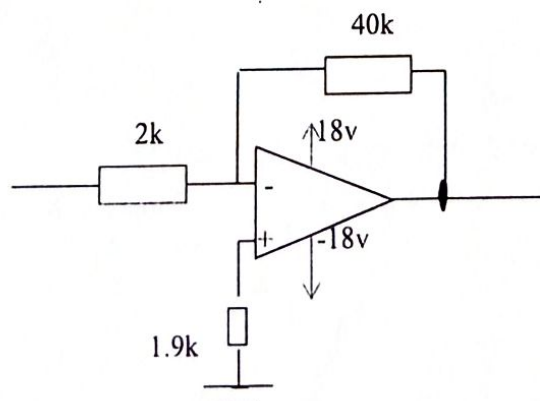

Question 6

- a) With aid of a labelled diagram explain the operation of a feedback circuit. (5mks)
- b) i) State a major reason why positive feedback is un-desirable in amplifiers. (2mks)
- ii) With reference to one application of positive feedback, demonstrate the conditions necessary for it to occur. (3mks)
- c) i) With suitable equations describe a negative feedback. (2mks)
- ii) State one fundamental characteristic of negative feedback amplifier. (1mk)
- iii) Identify any three advantages of negative feedback in amplifiers. (3mks)
- d) i) Distinguish between series and shunt- feedback circuits. (2mks)
- ii) Draw a circuit diagram showing a series feedback amplifier. (2mks)

Question 7

- a) i) what is a logic gate? (1mk)
- ii) Name the three basic gates and draw their circuit symbol. (3mks)
- iii) Explain the term truth table with the characteristics of its components. (3mks)
- b) i) write down the logic equations for the following gates AND, OR, NOT. Assume two inputs A and B for the AND and OR gates. (3mks)
- ii) Consider three input signals A, B and C, generate a truth table of their AND & OR gates. (5mks)
- iii) Draw the truth tables for the following gates NAND, NOR and EXOR with two inputs A and B. (5mks)

Question 8

- a) i) what is Boolean algebra. (1mk)
- ii) State any five laws of Boolean algebra. (5mks)
- iii) State how the laws mentioned in a) ii) can be proved. (2mks)
- iv) Use the mentioned approaches in a) iii) above with three input signals A, B & C to prove the distributive law. (8mks)
- c) Determine the simplest form of the following.
- i) $F = \bar{A}B + AB + A\bar{B} + AB$ (2mks)
- ii) $G = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C + ABC$ (2mks)